



**Electrical and Computer Engineering Department**  
**Digital Circuit Design II Lab : (10636391)**  
**Report Grading Sheet**

<b>Instructor Name: Dr. Ashraf Armoush</b>	<b>Experiment #: 3</b>		
<b>Academic Year: 2024/2025</b>	<b>Performed on: 22/2/2024</b>		
<b>Semester: 2st semester</b>	<b>Submitted on:</b>		
<b>Student Names:</b>			
1-Ahmad Ashayer	2-Asem Diab		
3-	4-		
5-	6-		
Evaluation Criterion	CLO	Grade	Points
<b>Abstract and Aims</b> Aims and idea of the experiment are clearly stated in simple words		10	
<b>Introduction, Apparatus and Procedures</b> Introduction is complete and well-written, all grammar/spelling correct, Appropriate background information related to the principles of the experiment is provided. The list of apparatus and procedures are also provided		15	
<b>Experimental Results, Calculations and Discussion</b> Results analyzed correctly. Experimental findings adequately and specifically summarized, in graphical, tabular, and/or written form. Comparison of theoretical predictions to experimental results, including discussion of accuracy and error analysis as needed.		50	
<b>Conclusions</b> Conclusions summarize the major findings from the experimental results with adequate specificity. Highlighting the most important results		15	
<b>Appearance</b> Title page is complete, page numbers applied, content is well organized, correct spelling, fonts are consistent, good visual appeal. You have also to use reference for the information you provide		10	
<b>Total</b>		100	

## -Abstract and Aims-

This experiment has four parts, all of them implemented in verlog, the first one is designing 4-bit Asynchronous counter by designing four T-Flip Flops, second one is designing 4-bit Synchronous updown counter, additionally for these two parts we need to design clock divider, for the third part designing button debouncing to use it as a trigger for updown counter, finally designing two digit BCD counter and show the digits by using two 7-segments display, for this part also it needed decoder and time multiplexer.


## -Introduction-

### 4-bit Asynchronous Up Counter

First for this part designing this counter needs four T-Flip Flops and this is the truth table for it:-

T	Clear	Q
X	0	0
0	1	Q
1	1	$\sim Q$

 And this is the figure for the Asynchronous counter:-




## Clock Divider

This circuit for the design clock, it take the clock as input and decrease it's frequency as output, and for this part the clock frequency is 100MHz and the output clock is 1Hz, so for some calculations the output of the counter which is maximum value will be 50M




## Top-Level Module

 
 
## 4-bit Synchronous Auto Updown Counter


For this second part, the implemented Synchronous counter has up and down situations, so it implemented by using arithmetic operators like + and − , and for this part it designed in behavioral description, and also as before it used the clock divider module for decreasing the frequency for the input clock as shown in the **top level module**:-


 
## Push Button UpDown Counter


For this part we implemented the counter but with additional part which is push button for controlling the counter, but before that there is one single problem with this circuit which is **Bouncing**, this appears when clicking on button there is a noise that making an effect to the

design, and to solve this issue we make a software debouncing solution to avoid this noise, and this is the module for this circuit:-



It takes two input and gives one output, for this solution, inside this block we determine the interval for that noise and simple making some delay for solving the issue.

 Finally this is the top-level module for that counter:-



## Two-Digit BCD Counter

For this final part, the BCD counter includes many blocks, some of them like Clock-Divider and this block has been implemented both in Asynchronous and Synchronous counters, and also it needs some additional blocks each one has its objective.

## BCD Counter

This digital circuit has counter from 0 to 9, but in this part we need to show the counter between 00 and 99, for the up situation, when the first digit reaches 9, the second digit incremented by 1 and the first will be 0.

And for the down situation when the first digit reaches 0, the second one will be decremented by one and the first one will be 9.



## Time Multiplexer

This digital circuit for displaying each digit in the same time, it takes the two digits as inputs and gives two output, one of them is the BCD digit itself, the other is Digit selector.


## BCD to 7-segment Decoder

This circuit for decode the 4 bit digit counter to 7 outputs each one is related to the 7-segment display.

And this is the truth table that needed for this part of experiment:-

	A	B	c	d	e	f	g
0	1	1	1	1	1	1	0
1	0	1	1	0	0	0	0
2	1	1	0	1	1	0	1
3	1	1	1	1	0	0	1
4	0	1	1	0	0	1	1
5	1	0	1	1	0	1	1
6	1	0	1	1	1	1	1
7	1	1	1	0	0	0	0
8	1	1	1	1	1	1	1
9	1	1	1	0	0	1	1
defalut	0	0	0	0	0	0	0

## Top-Level Module

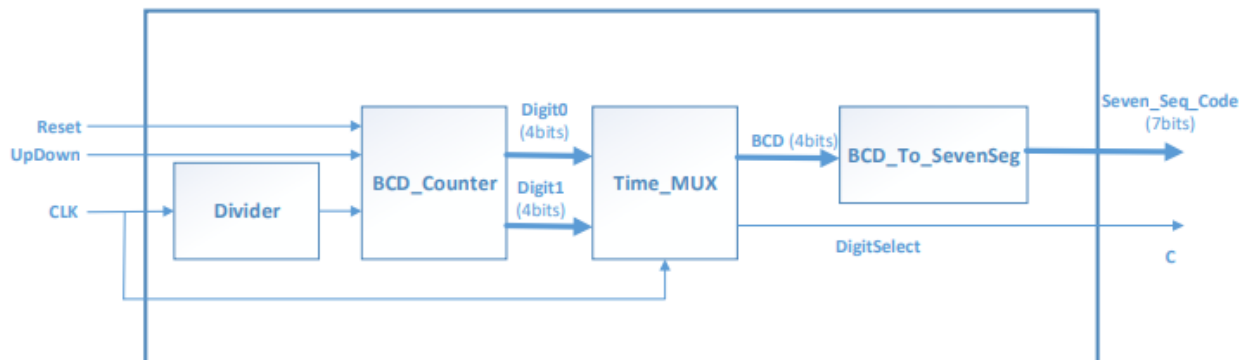



## - Experimental Results –

### Part one : 4-bit Asynchronous Up Counter

#### Code:

```
1 module TFF(  
2     input T,  
3     input Clk,  
4     input Reset,  
5     output reg Q,  
6     output reg Qbar  
7 );  
8 always@(posedge Clk,negedge Reset)  
9 begin  
10     if(Reset==0)  
11     begin  
12         Q<=0;  
13         Qbar<=1;  
14     end  
15     else if(T==1)  
16     begin  
17         Q<=~Q;  
18         Qbar=~Qbar;  
19     end  
20 end  
21 endmodule  
22
```

Figure 1: T Flip Flop

```
module AsyncCounter(  
    input Clk,  
    input Enable,  
    input Reset,  
    output [5:0] Q  
);  
    wire [6:0] clks;  
    assign clks[0]=Clk;  
    TFF TF1(Enable, clks[0], Reset, Q[0], clks[1]);  
    TFF TF2(Enable, clks[1], Reset, Q[1], clks[2]);  
    TFF TF3(Enable, clks[2], Reset, Q[2], clks[3]);  
    TFF TF4(Enable, clks[3], Reset, Q[3], clks[4]);  
    TFF TF5(Enable, clks[4], Reset, Q[4], clks[5]);  
    TFF TF6(Enable, clks[5], Reset, Q[5], clks[6]);  
endmodule
```

Figure 2 : Asyncous Counter



```
module ClkDivider(  
    input Clk,  
    output reg ClkOut  
);  
    integer Counter=0;  
    reg forClk=0;  
    always@(posedge Clk)  
  
    begin  
        Counter=Counter+1;  
        if(Counter==500000000)  
        begin  
            Counter=0;  
            forClk=~forClk;  
            ClkOut=forClk;  
        end  
    end  
endmodule
```

Figure 3 : Clock Divider

```
module TopLevelR(  
    input Reset,  
    input Enable,  
    input Clk,  
    output [5:0] Q  
);  
    wire ClkOut;  
    ClkDivider uut1(Clk, ClkOut);  
    AsyncCounter uut2(ClkOut, Enable, Reset,  
endmodule
```

Figure 4 : Top Level

## Testbench:



```
`timescale 1ns / 1ps
module AsyncCounter_tb(


);
    integer i;
    reg Reset;
    reg Clk;
    reg Enable;
    wire [5:0]Q;
begin
    Clk<=0;
    for(i=0;i<4000;i=i+1)
    begin
        #10;Clk<=~Clk;
    end
end

    AsyncCounter uut (Clk,Enable,Reset,Q);
begin
    #10;
    Enable<=0;
    Reset<=0;
    #20;
    Enable<=1;
    #30;
    Reset<=1;
    #500;

end
endmodule
```

Figure 5 : testbench of async counter

**Wave :**

 

**Part two :** 4-bit synchronous Up/down Counter



```

module syncCount (
    input Clk,
    input UpDown,
    input Reset,
    output reg [3:0] Q
);
    always@(posedge Clk,negedge Reset)
    begin
        if(Reset==0)
        begin
            Q=0;
        end
        else if(UpDown==0)
        begin
            Q<=Q+1;
        end
        else
        begin
            Q<=Q-1;
        end
    end
endmodule

```

Figure 6 : syncrous up/down counter

```
module TopLevelForSync(
    input Clk,
    input UpDown,
    input Reset,
    output [3:0] Q
);
    wire ClkOut;
    ClkDivider uut1(Clk, ClkOut);
    syncCount uut2(ClkOut, UpDown, Reset, Q);
endmodule
```

Figure 7: top level module

```

`timescale 1ns / 1ps

module syncCount_tb();

    integer i;
    reg Reset;
    reg Clk;
    reg UpDown;
    wire [3:0]Q;
    initial begin
        Clk<=0;
        for(i=0;i<4000;i=i+1)
            begin
                #10;Clk<=~Clk;
            end
        end

        syncCount uut (Clk,UpDown,Reset,Q);
        initial begin
            #10;
            UpDown<=0;
            Reset<=0;
            #20;
            UpDown<=1;
            Reset<=1;
            #500;
            UpDown<=0;
            #30;

        end
    endmodule

```

Figure 8: testbench

 


Figure 9: wave of summation



## Part three : Push Button UpDown Counter

```

module PBDebounce(
    input Clk,
    input PB,
    output reg PBOut
);
    reg Ton=0;
    reg Old=0;
    integer count=0;
    integer max=1000000;
    always@(posedge Clk)
    begin
        if(Ton==0)
        begin
            if(PB!=Old)
            begin
                Ton<=1;
                count=0;
                Old<=PB;
            end //end for if (P
        end//end for Ton==0
        else
        begin
            count=count+1;
            if(count==max)
            begin
                Ton=0;
                PBOut<=~PBOut;
            end //for count==max
        end //for Ton==1
    end//for always
endmodule

```

Figure 10 : push button debouncer

```

module syncCount(
    input Clk,
    input UpDown,
    input Reset,
    output reg [3:0] Q
);
    always@(posedge Clk,negedge Reset)
    begin
        if(Reset==0)
        begin
            Q=0;
        end
        else if(UpDown==0)
        begin
            Q<=Q+1;
        end
        else
        begin
            Q<=Q-1;
        end
    end
endmodule

```

Figure 11:synchronous counter implementation

```

module TopLevelForPB(
    input Reset,
    input UpDown,
    input Clk,
    input PB,
    output [3:0] Q
);
    wire PBOut;
    PBDebounce uut1(Clk,PB,PBOut);
    syncCount uut2(PBOut,UpDown,Reset,Q);
endmodule

```

Figure 12 : top level of part 3

## Part 4: Two-Digit BCD Counter



```

`timescale 1ns / 1ps
) module BCD_tb();
    reg Reset;
    reg Clk=0;
    reg UpDown;
    wire [3:0]dig0;
    wire [3:0]dig1;
    BCDCounter uut(Reset,UpDown,Clk,dig0,dig1);
)    initial begin
)    forever begin
#1; Clk=~Clk;
)    end
)    end
    initial begin
        #10;
        Reset<=0;
        UpDown<=0;
        #20;
        Reset<=0;
)    UpDown<=1;

        #20;
        Reset<=1;
        UpDown<=0;
        #210;
        UpDown<=1;
        Reset<=1;
        #200;
    end
) endmodule

module TDM(
    input Clk,
    input [3:0] Dig0,
    input [3:0] Dig1,
    output reg [3:0] DigOut,
    output reg DigitSelect
);
    integer counter=0;

    always@(posedge Clk)
    begin
        if(DigitSelect==0)
        begin
            DigOut<=Dig0;
        end
        else
        begin
            DigOut<=Dig1;
        end

        counter=counter+1;
        if(counter==1000000)
        begin
            counter=0;
            DigitSelect<=~DigitSelect;
        end
    end
endmodule

```




```

module BCDCounter(input Reset,
    input UpDown, input Clk,
    output reg [3:0] Dig0,
    output reg [3:0] Dig1 );
always@(posedge Clk, negedge Reset)
begin
    if(Reset==0)
    begin
        Dig0<=0;
        Dig1<=0;
    end// foooooor reset
    else
    begin
        if(UpDown==0)
        begin
            if(Dig0==9)
            begin
                Dig0=0;
            end
            if(Dig1==9)
            begin
                Dig1=0;
            end
        end //for dig1==9
    end
    else
    begin
        Dig0=Dig0+1;
    end //for if updown==0
    else
    begin
        if(Dig0==0)
        begin
            Dig0=9;
        end
        if(Dig1==0)
        begin
            Dig1=9;
        end
        else
        begin
            Dig1=Dig1-1;
        end //for Dig0==0
        else
        begin
            Dig0=Dig0-1;
        end //foooooor upDown=1
    end //foooooor else (UpDown)
    end //foooooor always
endmodule

module Decoder(
    input [3:0] Digit,
    output reg AA,
    output reg AB,
    output reg AC,
    output reg AD,
    output reg AE,
    output reg AF,
    output reg AG
);
always@(Digit)
begin
    case(Digit)
    0: {AA, AB, AC, AD, AE, AF, AG} <= 7'b1111110;
    1: {AA, AB, AC, AD, AE, AF, AG} <= 7'b0110000;
    2: {AA, AB, AC, AD, AE, AF, AG} <= 7'b1101101;
    3: {AA, AB, AC, AD, AE, AF, AG} <= 7'b1111001;
    4: {AA, AB, AC, AD, AE, AF, AG} <= 7'b0110011;
    5: {AA, AB, AC, AD, AE, AF, AG} <= 7'b1011011;
    6: {AA, AB, AC, AD, AE, AF, AG} <= 7'b1011111;
    7: {AA, AB, AC, AD, AE, AF, AG} <= 7'b1110000;
    8: {AA, AB, AC, AD, AE, AF, AG} <= 7'b1111111;
    9: {AA, AB, AC, AD, AE, AF, AG} <= 7'b1110011;
    default: {AA, AB, AC, AD, AE, AF, AG} <= 7'b0000000;
    endcase
end
endmodule

module topLevel(
    input Reset,
    input UpDown,
    input Clk,
    output AA,
    output AB,
    output AC,
    output AD,
    output AE,
    output AF,
    output AG,
    output c
);
    wire ClkOut;
    wire [3:0] Dig0;
    wire [3:0] Dig1;
    wire [3:0] BCD;
    ClkDivider uut1(Clk, ClkOut);
    BCDCounter uut2(Reset, UpDown, ClkOut, Dig0, Dig1);
    TDM uut3(Clk, Dig0, Dig1, BCD, c);
    Decoder uut4(BCD, AA, AB, AC, AD, AE, AF, AG);
endmodule

```

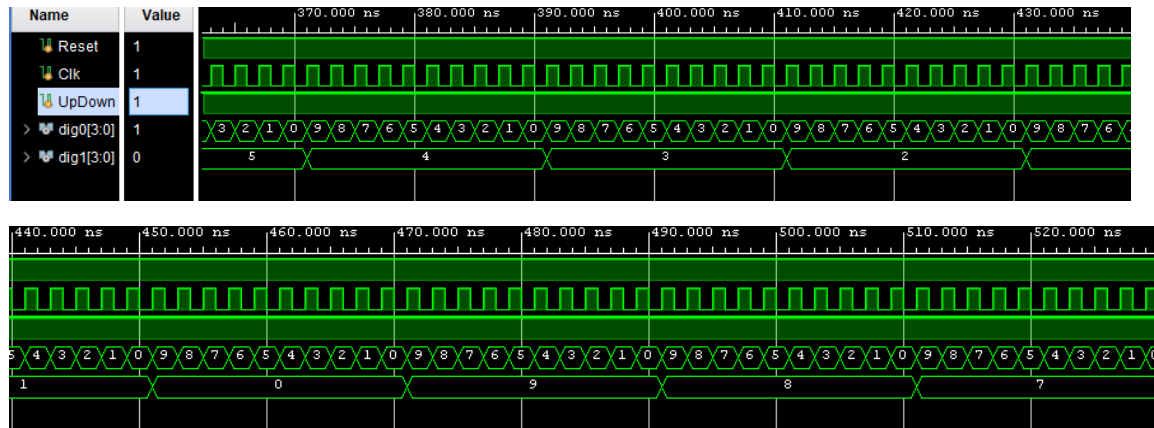

## Conclusions -

In this experiment we learned how to implement asynchronous counter by using flips-flops circuit, and also implementing synchronous counter and for both we implemented clock divider for the system design clock,

Also we learned how to deal with bouncing problem in the lap and solving the noise issue when we use push button,

Finally we learned how to make BCD counter and how to show it in multiple 7-segments display.